

---

# ECE M116C / CS 151B: Week 2

## Section

---

Justin Feng

## RV32I Base Instruction Set (MIT 6.004 subset)

imm[31:12]				rd	0110111
imm[20:10:11:19:12]				rd	1101111
imm[11:0]		rs1	000	rd	1100111
imm[12:10:5]	rs2	rs1	000	imm[4:1:11]	1100011
imm[12:10:5]	rs2	rs1	001	imm[4:1:11]	1100011
imm[12:10:5]	rs2	rs1	100	imm[4:1:11]	1100011
imm[12:10:5]	rs2	rs1	101	imm[4:1:11]	1100011
imm[12:10:5]	rs2	rs1	110	imm[4:1:11]	1100011
imm[12:10:5]	rs2	rs1	111	imm[4:1:11]	1100011
imm[11:0]		rs1	010	rd	0000011
imm[11:5]	rs2	rs1	010	imm[4:0]	0100011
imm[11:0]		rs1	000	rd	0010011
imm[11:0]		rs1	010	rd	0010011
imm[11:0]		rs1	011	rd	0010011
imm[11:0]		rs1	100	rd	0010011
imm[11:0]		rs1	110	rd	0010011
imm[11:0]		rs1	111	rd	0010011
0000000	shamt	rs1	001	rd	0010011
0000000	shamt	rs1	101	rd	0010011
0100000	shamt	rs1	101	rd	0010011
0000000	rs2	rs1	000	rd	0110011
0100000	rs2	rs1	000	rd	0110011
0000000	rs2	rs1	001	rd	0110011
0000000	rs2	rs1	010	rd	0110011
0000000	rs2	rs1	011	rd	0110011
0000000	rs2	rs1	100	rd	0110011
0000000	rs2	rs1	101	rd	0110011
0100000	rs2	rs1	101	rd	0110011
0000000	rs2	rs1	110	rd	0110011
0000000	rs2	rs1	111	rd	0110011

LUI  
 JAL  
 JALR  
 BEQ  
 BNE  
 BLT  
 BGE  
 BLTU  
 BGEU  
 LW  
 SW  
 ADDI  
 SLTI  
 SLTIU  
 XORI  
 ORI  
 ANDI  
 SLLI  
 SRLI  
 SRAI  
 ADD  
 SUB  
 SLL  
 SLT  
 SLTU  
 XOR  
 SRL  
 SRA  
 OR  
 AND

31	25	24	20	19	15	14	12	11	7	6	0		
funct7			rs2		rs1		funct3		rd		opcode		R-type
imm[11:0]					rs1		funct3		rd		opcode		I-type
imm[11:5]			rs2		rs1		funct3		imm[4:0]		opcode		S-type
imm[12:10:5]			rs2		rs1		funct3		imm[4:1:11]		opcode		B-type
			imm[31:12]						rd		opcode		U-type
			imm[20:10:11:19:12]						rd		opcode		J-type

## Ex) Machine Code for JAL

---

-Write the machine code for: jal ra, -896

# Ex) Machine Code for JAL

-Write the machine code for: jal ra, -896

**Ans:**

--86 to binary (two's complement):

11111111110010000000

20<sup>th</sup> bit -> 1

10:1 -> 1001000000


11<sup>th</sup> bit -> 1


19:12 -> 11111111

11001000000111111111 00001 1101111



# Von Neuman Model

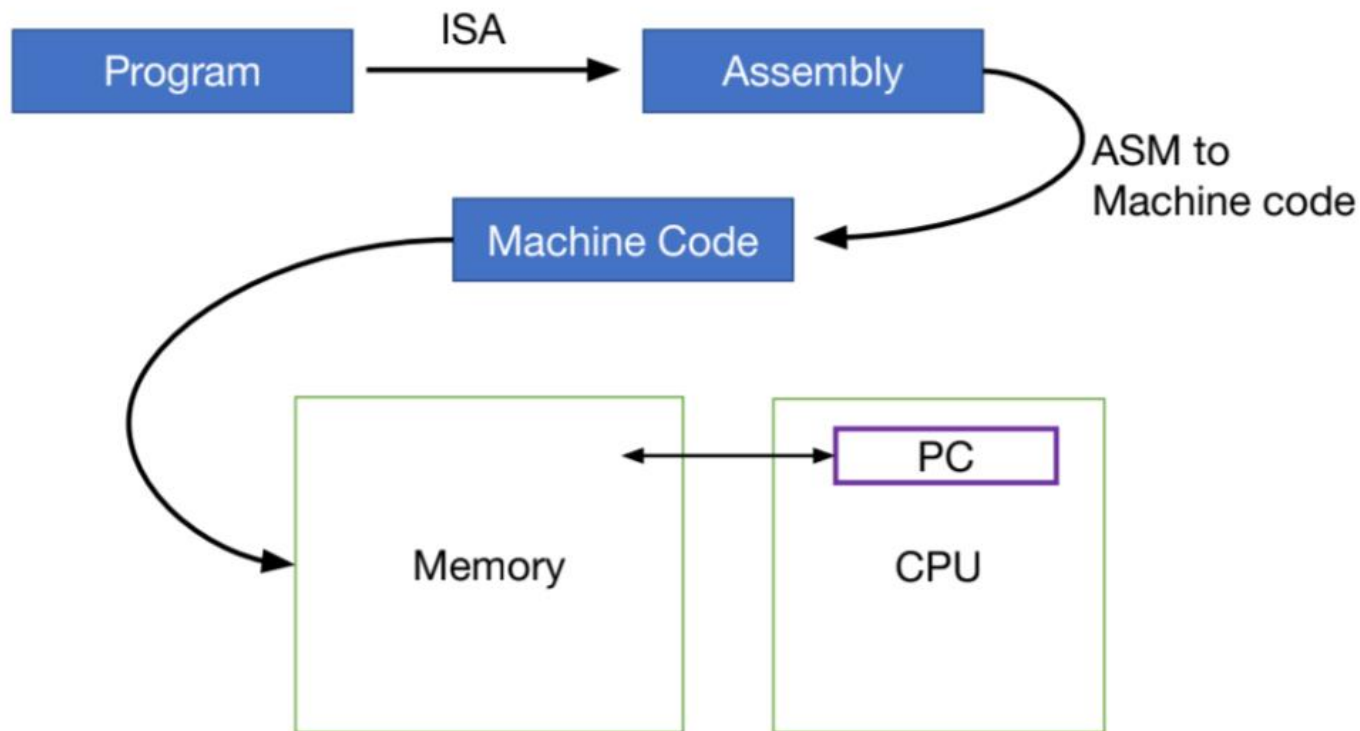

 

## Datapath + Controller


\*Images were taken from Hennessy Patterson Book [1].

# Single Cycle CPU

# Steps in a CPU

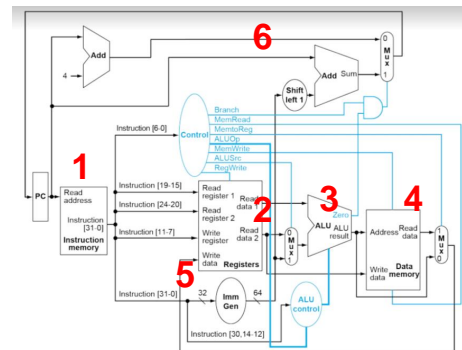- 1) Fetch Instruction
- 2) Decode (register)
- 3) Execution (ALU)
- 4) Memory
- 5) Writeback
- 6) Update PC

-In single cycle cpu, all these steps finish in one cycle!  
-Note: order of steps does not indicate in which order they finish



\*Images were taken from Hennessy Patterson Book [1].


Datapath +  
Controller



# Datapath
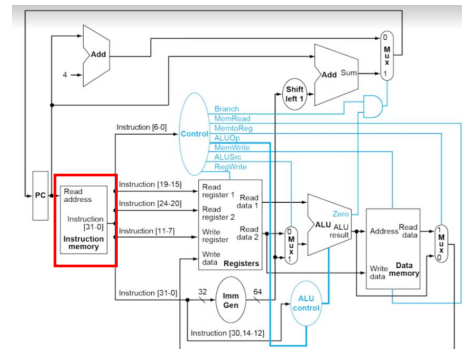
# Instruction Memory

- Stores each of our 32 bit instructions
- PC indexes into instruction memory
- PC + 4: the next instruction
- PC + Offset: the instruction to access after a jump/branch




\*Images were taken from Hennessy Patterson Book [1].

Datapath +  
Controller

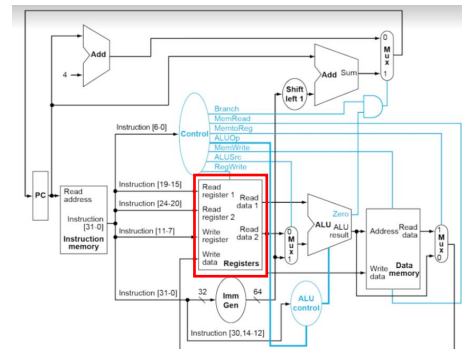
# Register File

- Stores our 32 registers of size 32 bits each for easy access/write.
- Different instruction bits go to different ports
- RS1 address, RS2 address, Rd address
- Address ports used to access values of specific registers
- Rd address specifies which register we should write to after our operation





Datapath +  
Controller

 \*Images were taken from Hennessy Patterson Book [1].


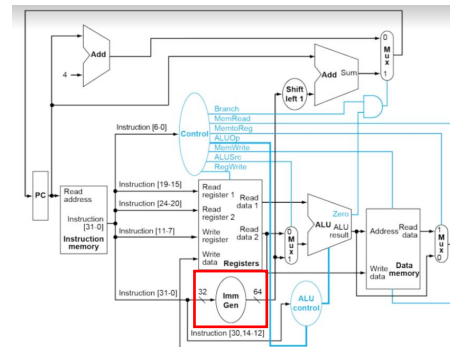 
# Imm Gen

- Given a 32 bit instruction, need to construct a 32 bit immediate
- Sign extension
- Use knowledge of full instruction to assign bits to bit positions





\*Images were taken from Hennessy Patterson Book [1].

Datapath +  
Controller
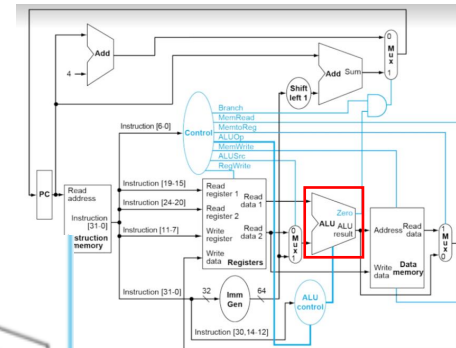 
# Arithmetic Logic Unit


- Does basic math operations
- Addition, subtraction, logical, etc
- Zero flag: if a branch condition is true, set the zero flag to true such that we know to branch
- ALU Control: used to select which operation to do



\*Images were taken from Hennessy Patterson Book [1].
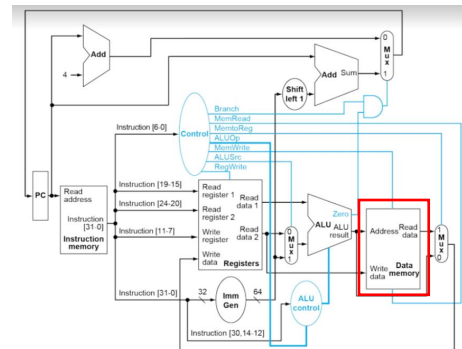
# Data Memory

- Stores data in longer term storage
- Byte addressable
- Accessed via loads, with result stored in register file
- Modified via stores, given an address (computed by ALU) and the data (from register file)




\*Images were taken from Hennessy Patterson Book [1].

Datapath +  
Controller
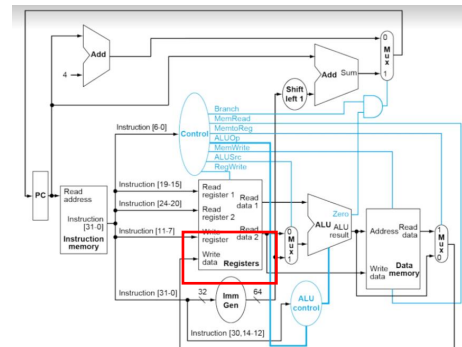
# Write Back

- Write back value to register file
- Store instruction: don't need to write back!
- Grab value from either data memory or ALU, place into register file




\*Images were taken from Hennessy Patterson Book [1].

Datapath +  
Controller

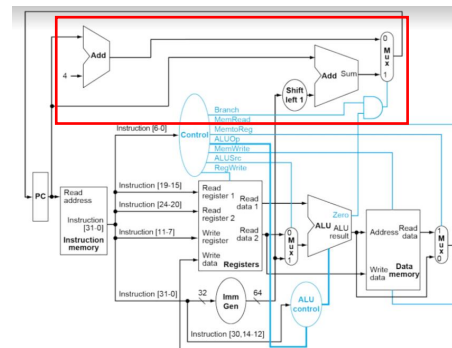
# PC Generation

- Compute next instruction to process
- Normal operation: add 4 to existing PC
- Branches/jumps: add offset to PC
  - Shift left by 1? Remember, zeroth bit missing in instruction. This also ensures even addresses
- Use mux to select correct PC value



Datapath +  
Controller

 \*Images were taken from Hennessy Patterson Book [1].






# Controller

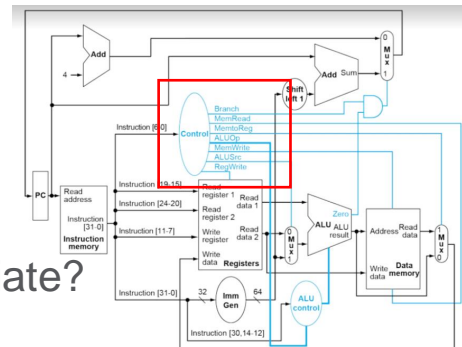
# Controller

- Oversight over datapath to do correct operation
- Questions answered:
  - Read/write from memory?
  - Place value from memory into register?
  - 2<sup>nd</sup> ALU operand being from register, or immediate?
  - Write into register file?
  - The exact ALU operation?
- Done via just the opcode




\*Images were taken from Hennessy Patterson Book [1].

Datapath +  
Controller

 

# Controller

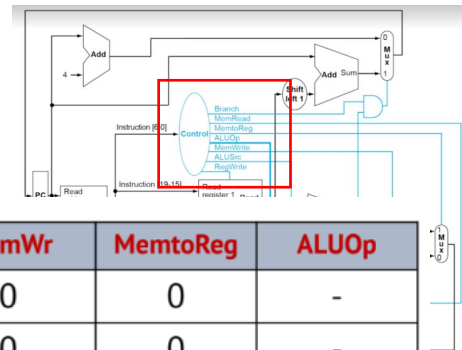

Datapath +  
Controller


Instruction	Opcode	RegWrite	AluSrc	Branch	MemRe	MemWr	MemtoReg	ALUOp
R-type	0110011	1	0	0	0	0	0	-
I-type	0010011	1	1	0	0	0	0	-
lw	0000011	1	1	0	1	0	1	-
sw	0100011	0	1	0	0	1	0	-
beq	1100011	0	0	1	0	0	0	-

# ALU Control

- Given an opcode, return a 2 bit value (what kind of instruction it is (ld, sd, beq, r type))
- Based on what instruction opcode it is (ALUOp) and the func codes, do the correct ALU operation (add, and, etc

Instruction opcode	ALUOp
ld	00
sd	00
beq	01
R-type	10
R-type	10
R-type	10
R-type	10

Funct7 field	Funct3 field	Desired ALU action	ALU control input
XXXXXXX	XXX	add	0010
XXXXXXX	XXX	add	0010
XXXXXXX	XXX	subtract	0110
0000000	000	add	0010
0100000	000	subtract	0110
0000000	111	AND	0000
0000000	110	OR	0001

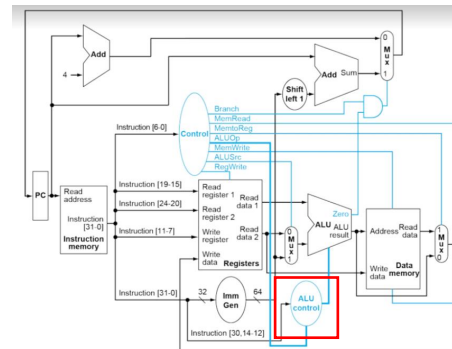

\*Images were taken from Hennessy Patterson Book [1].

Datapath +  
Controller

Note: there was some confusion over the naming of the output of the ALU control. We will call it “Operation”

## Ex) Add Instruction?


---

-How does an “add” instruction propagate through the datapath/controller?

add rd, rs1, rs2
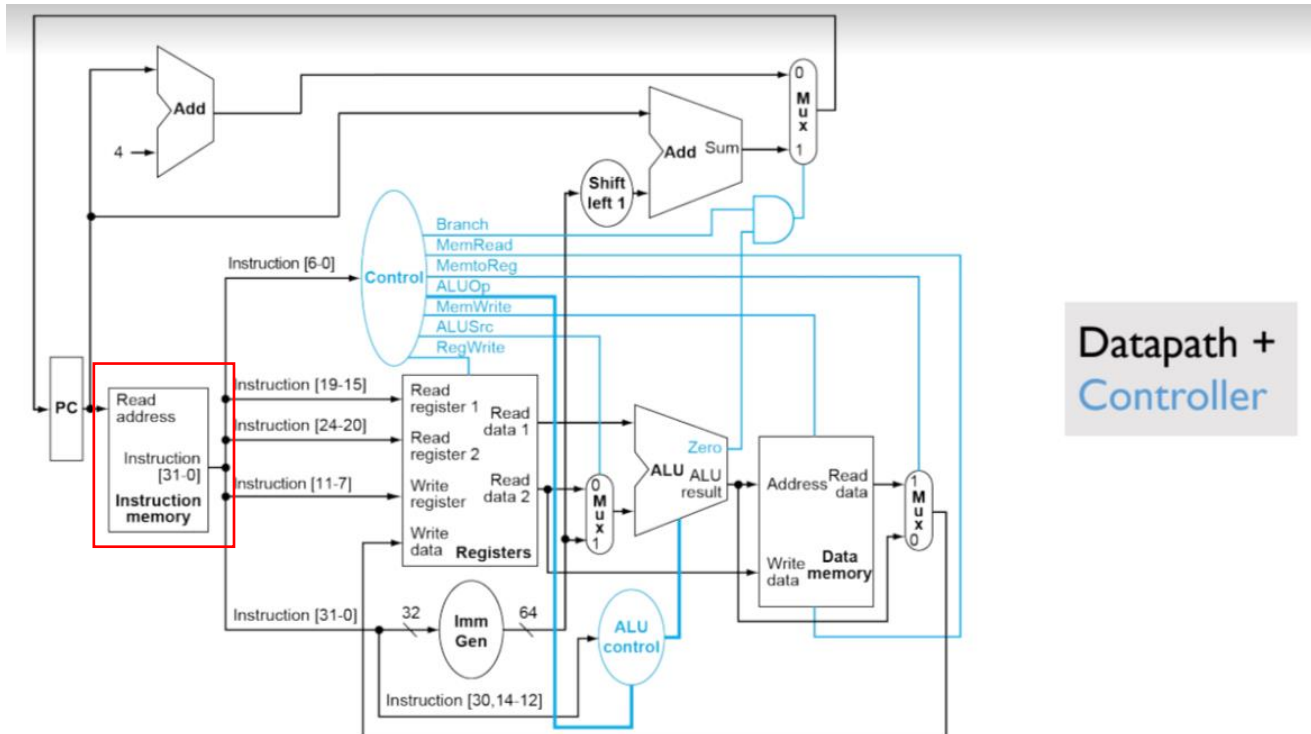
# Ex) Add Instruction?

-Grab instruction from instruction memory




Datapath +  
Controller

\*Images were taken from Hennessy Patterson Book [1].
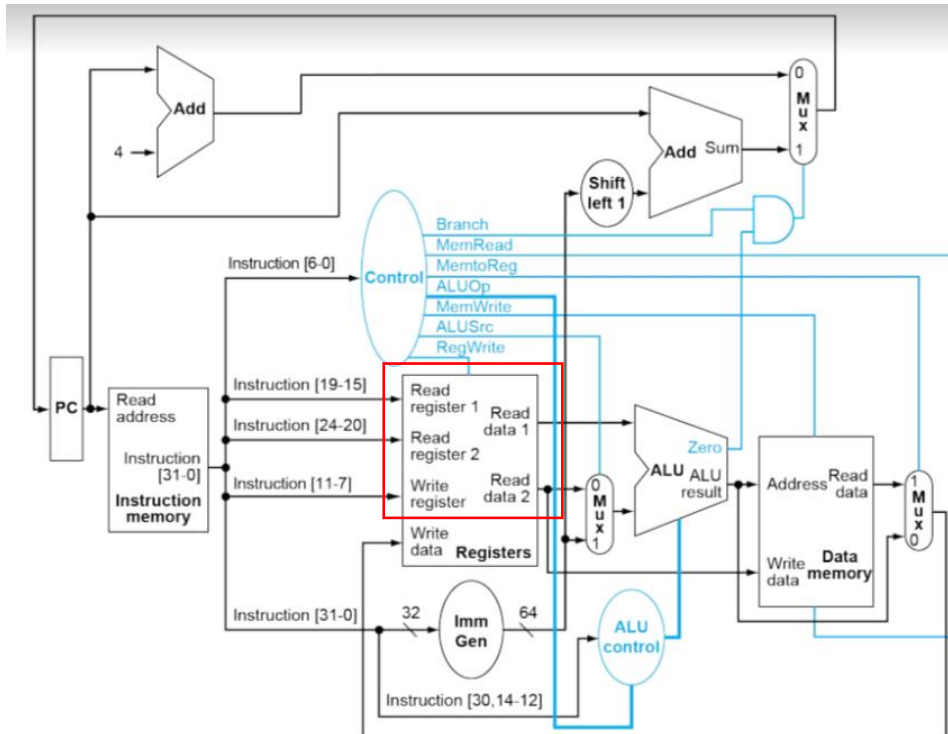
# Ex) Add Instruction?

-Access register values for operands, using register addresses found in instruction (rs1, rs2)




Datapath +  
Controller

\*Images were taken from Hennessy Patterson Book [1].
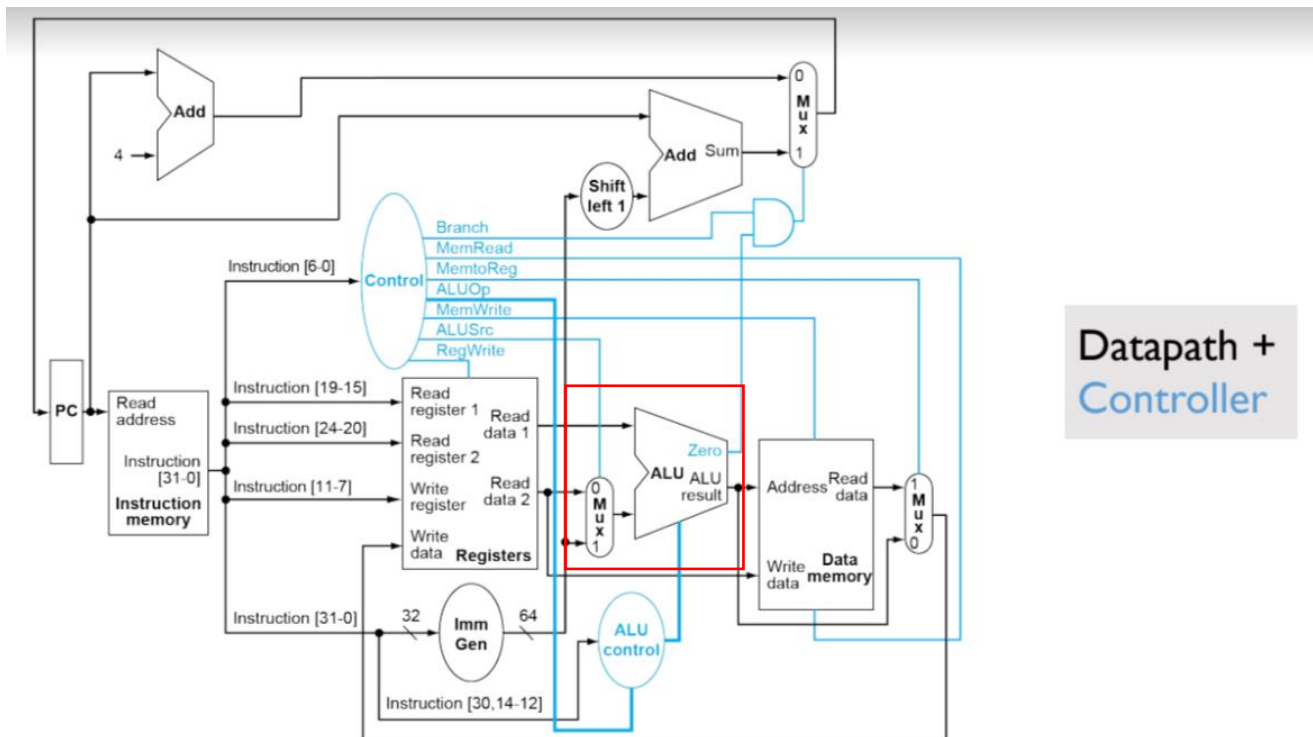
# Ex) Add Instruction?

- Select mux input 0 (read data 2)
- Add values in rs1 and rs2 together in ALU




Datapath +  
Controller

\*Images were taken from Hennessy Patterson Book [1].



# Ex) Add Instruction?

-Mem?  
Nothing!

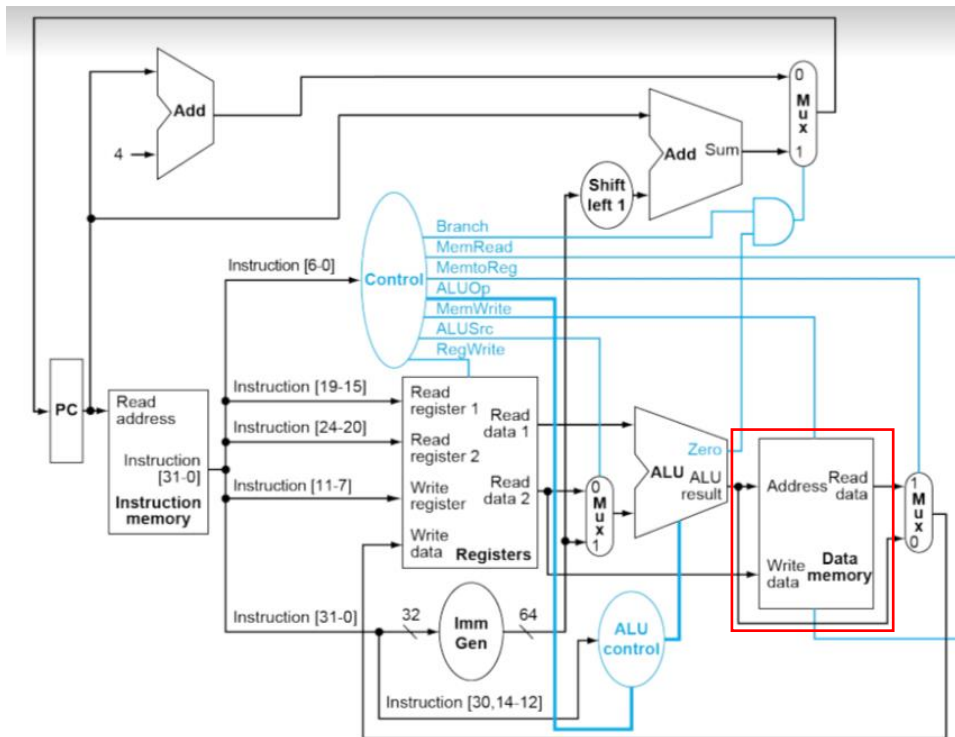


Datapath +  
Controller

\*Images were taken from Hennessy Patterson Book [1].
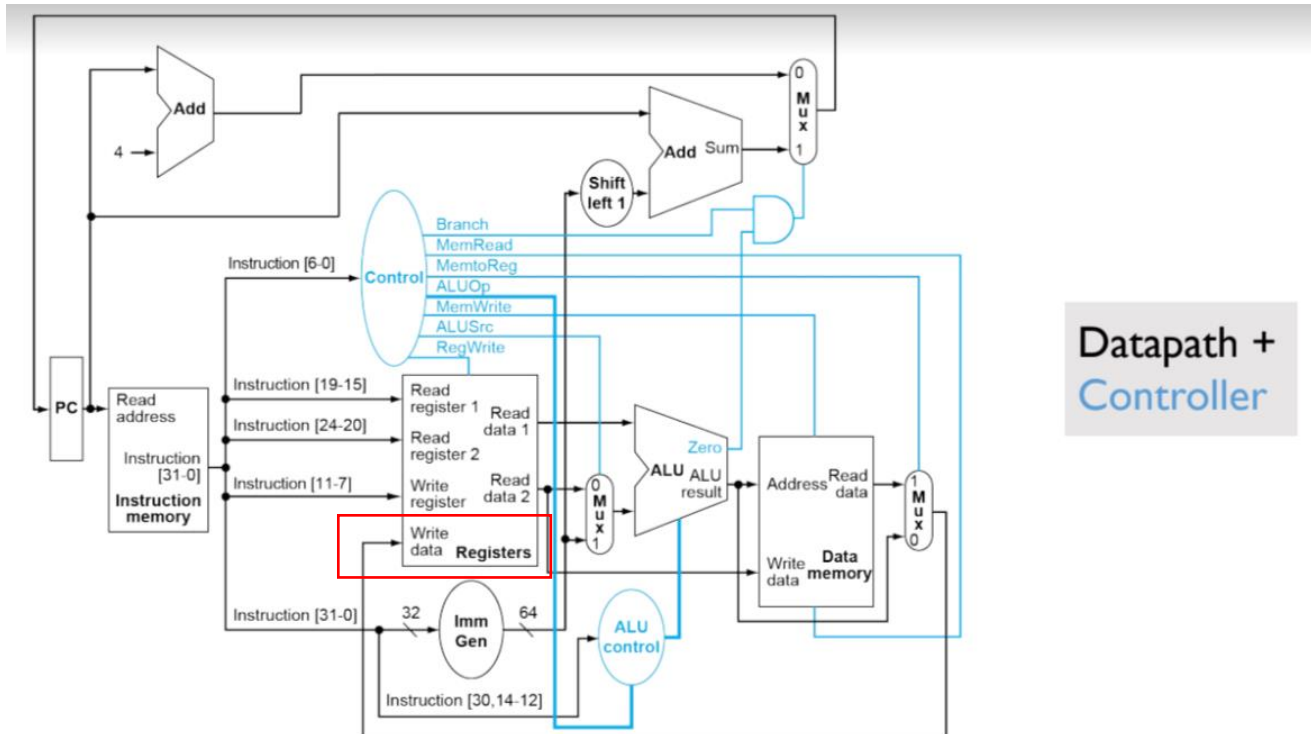
# Ex) Add Instruction?

-Write back  
to memory  
the sum,  
using  
address rd




Datapath +  
Controller

\*Images were taken from Hennessy Patterson Book [1].

## Ex) Add Instruction?

- PC gets updated!
- No branch

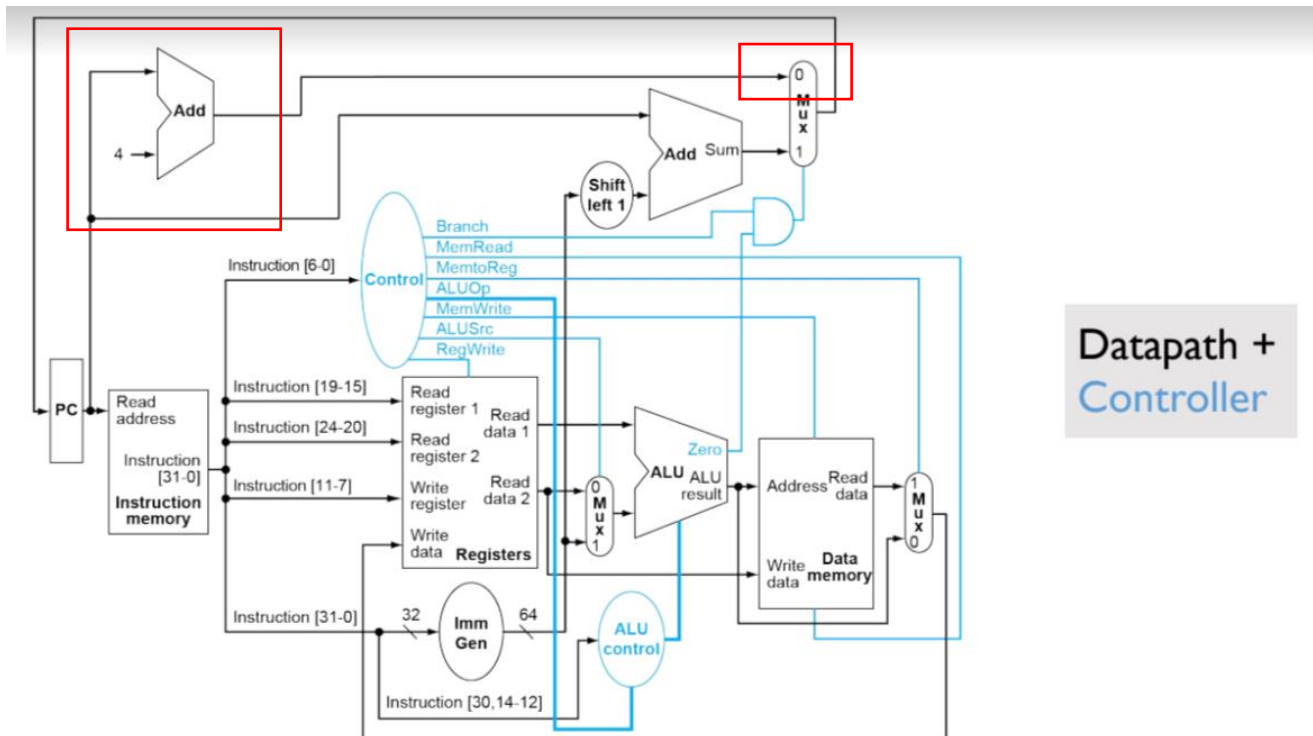


## Datapath + Controller

\*Images were taken from Hennessy Patterson Book [1].

# Ex) Add Instruction?

- Controller:
- Branch: 0
- MemRead: 0
- MemtoReg: 0
- ALUOp: 10
- MemWrite: 0
- ALUSrc: 0
- RegWrite: 1

-ALU control:  
0010

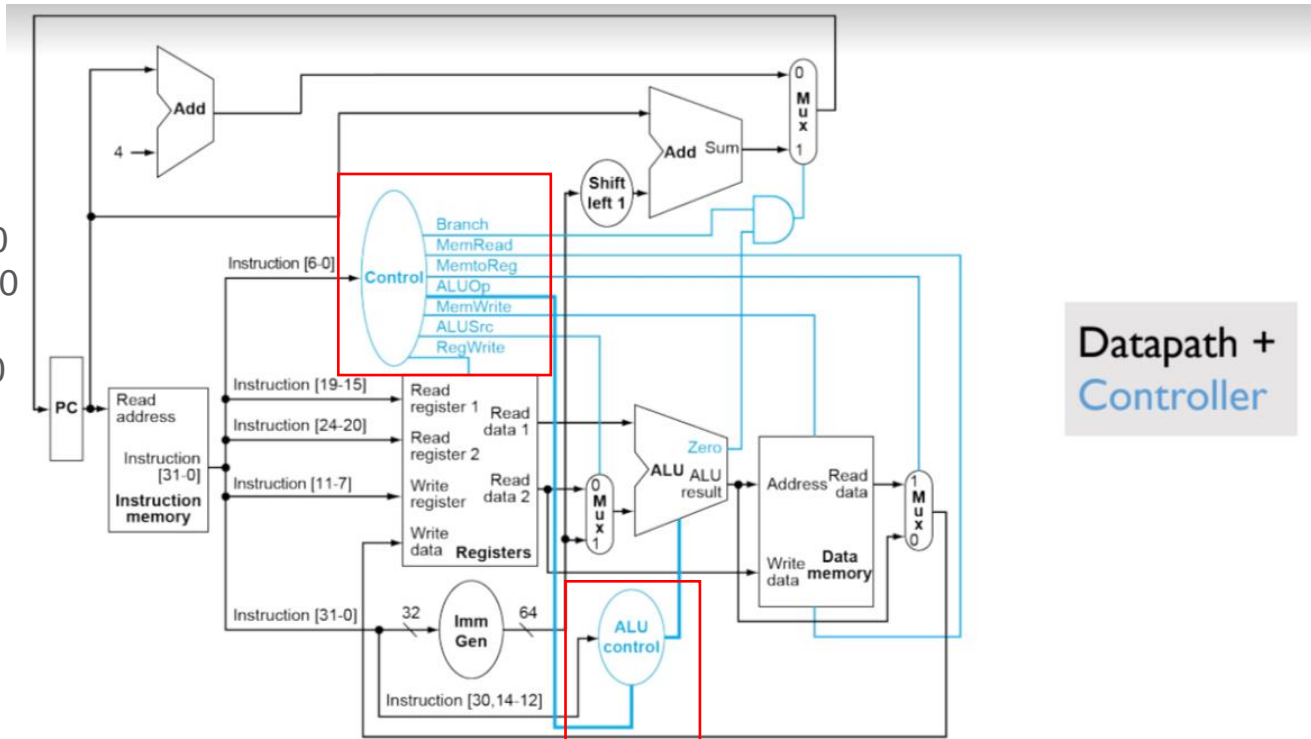

Datapath +  
Controller

\*Images were taken from Hennessy Patterson Book [1].

## Ex) Store Instruction?


---

-How does a “store” instruction propagate through the datapath/controller?

sw rs2, imm(rs1)
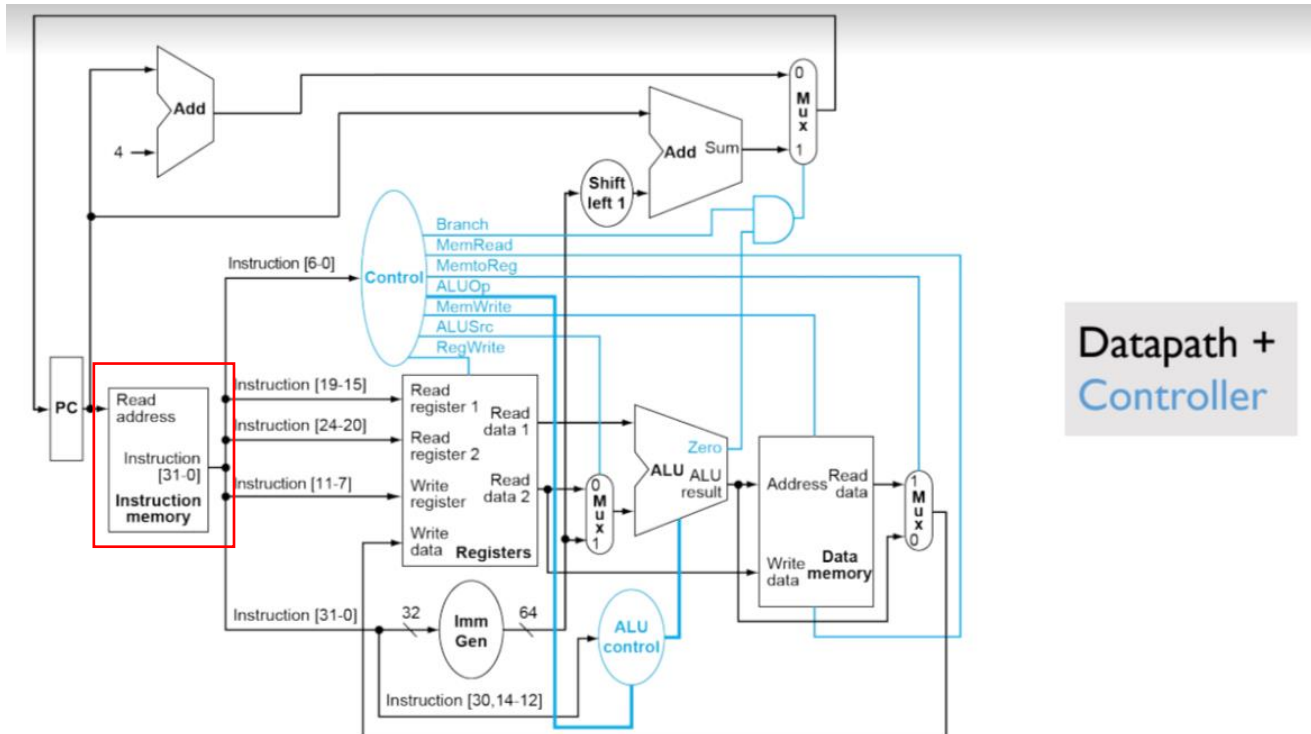
# Ex) Store Instruction?

-Grab instruction from instruction memory




Datapath +  
Controller

\*Images were taken from Hennessy Patterson Book [1].
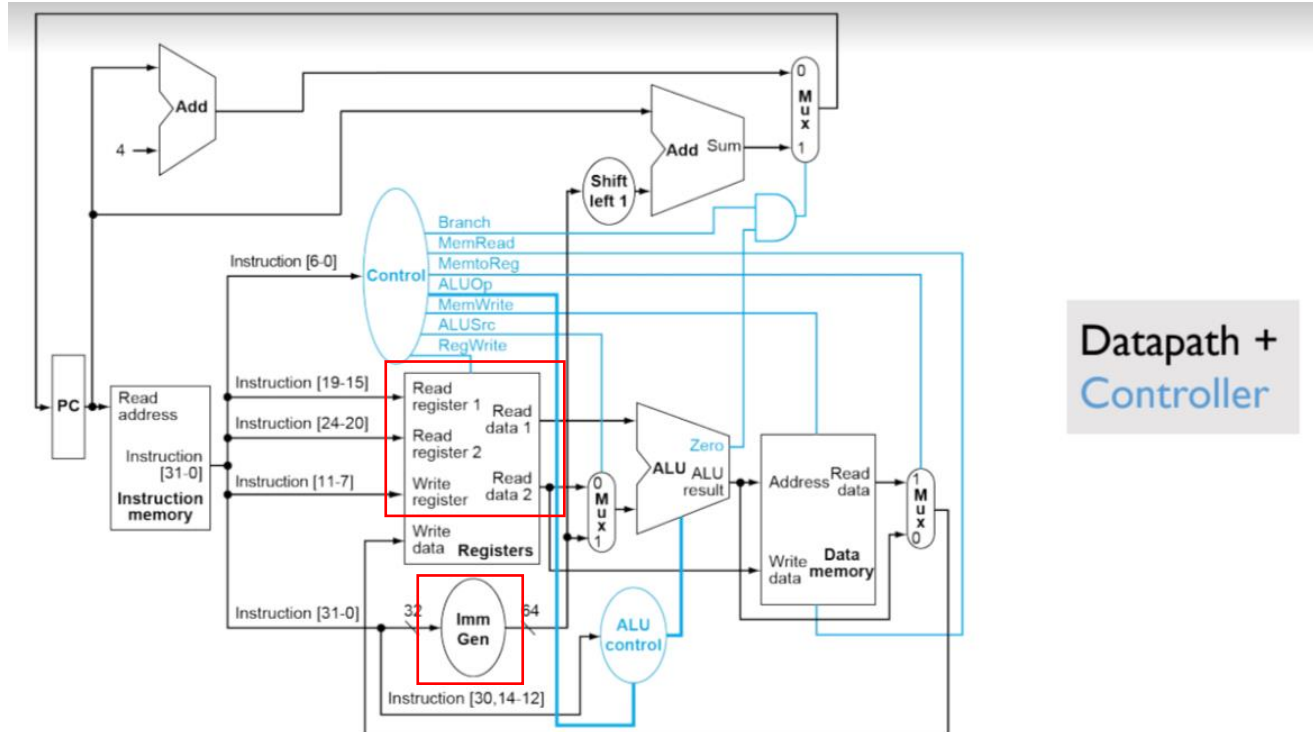
# Ex) Store Instruction?

- Access register values for operands, using register addresses found in instruction (rs1, rs2)
- Generate immediate




Datapath +  
Controller

\*Images were taken from Hennessy Patterson Book [1].
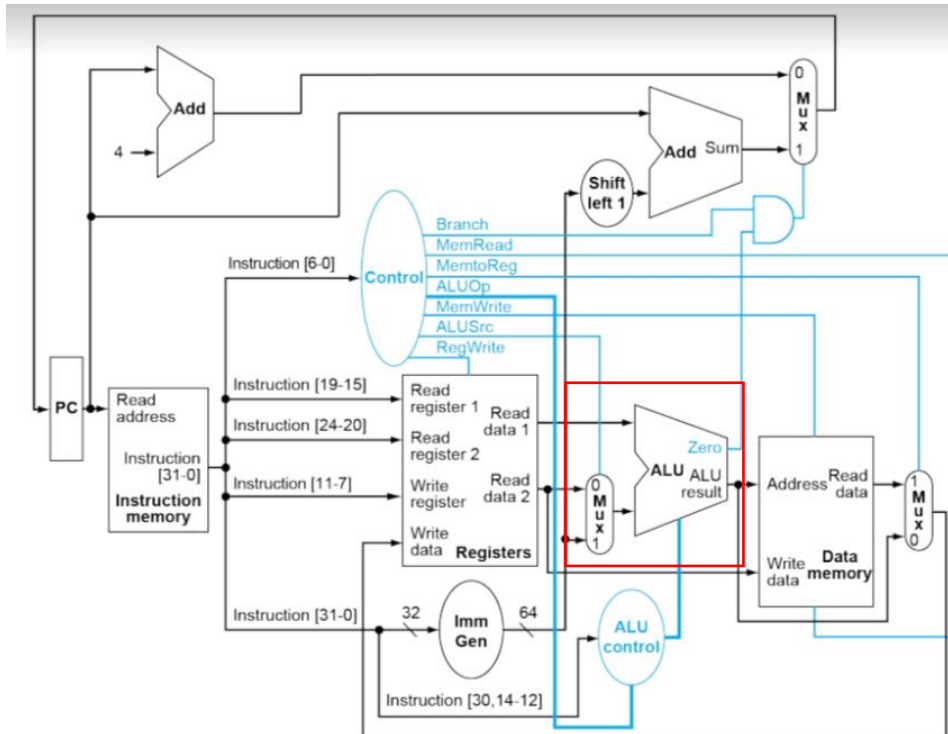
# Ex) Store Instruction?

- Select mux input 1 (immediate)
- Add values in rs1, and immediate together




Datapath +  
Controller

\*Images were taken from Hennessy Patterson Book [1].


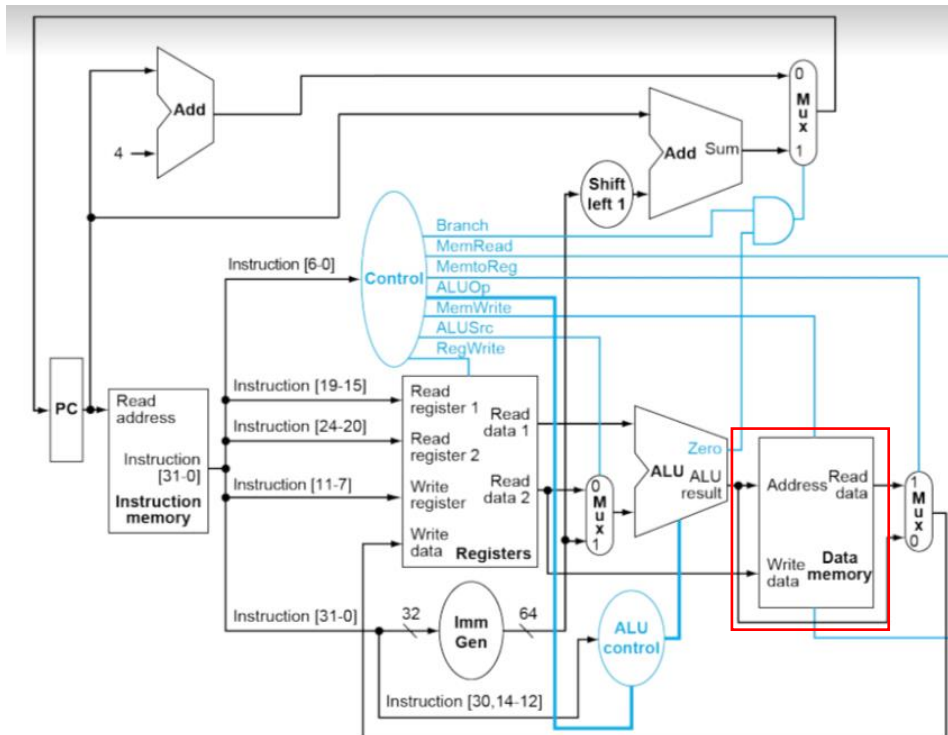
# Ex) Store Instruction?

-Using result of ALU, store value in rs2 into data memory (address of: value in rs1, + imm)




Datapath +  
Controller

\*Images were taken from Hennessy Patterson Book [1].

# Ex) Store Instruction?

-Write  
back?  
-Nope!

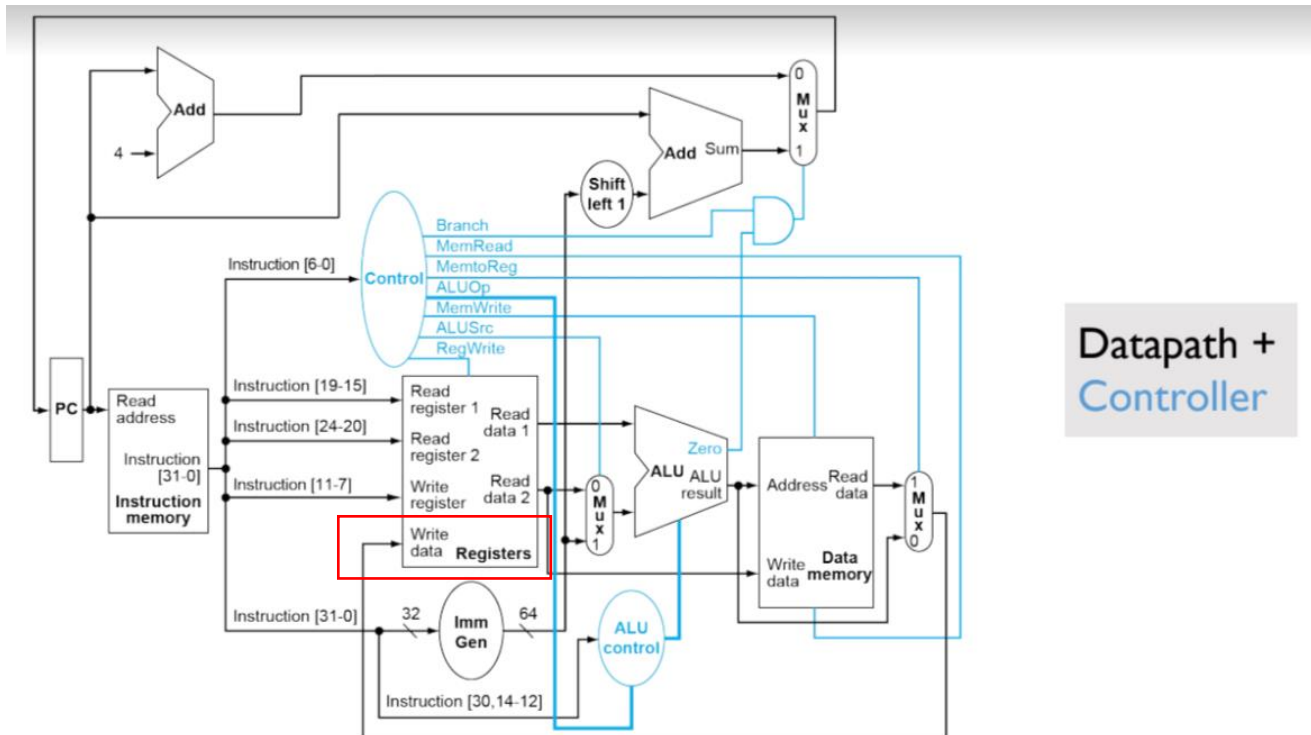


Datapath +  
Controller

\*Images were taken from Hennessy Patterson Book [1].

## Ex) Store Instruction?

- PC gets updated!
- No branch

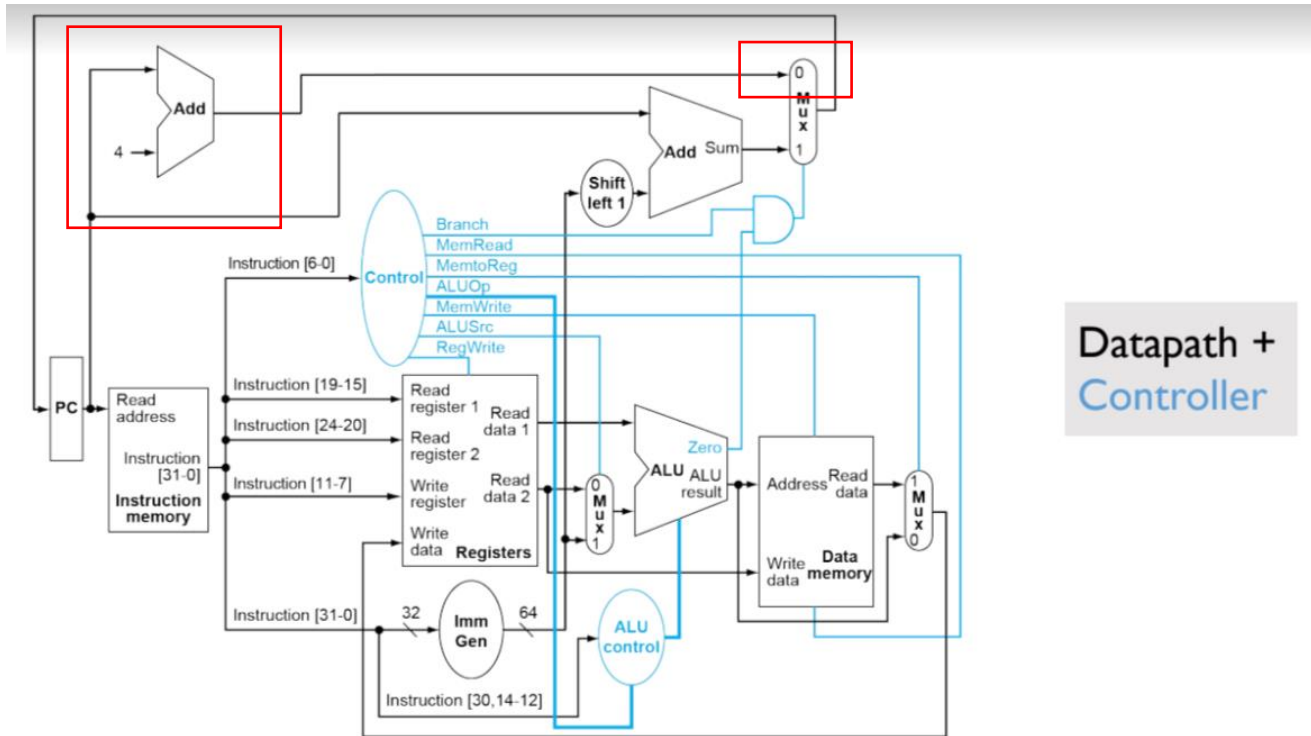


\*Images were taken from Hennessy Patterson Book [1].

# Ex) Store Instruction?

- Controller:
- Branch: 0
- MemRead: 0
- MemtoReg: 0
- ALUOp: 00
- MemWrite: 1
- ALUSrc: 1
- RegWrite: 0

-ALU control:  
0010

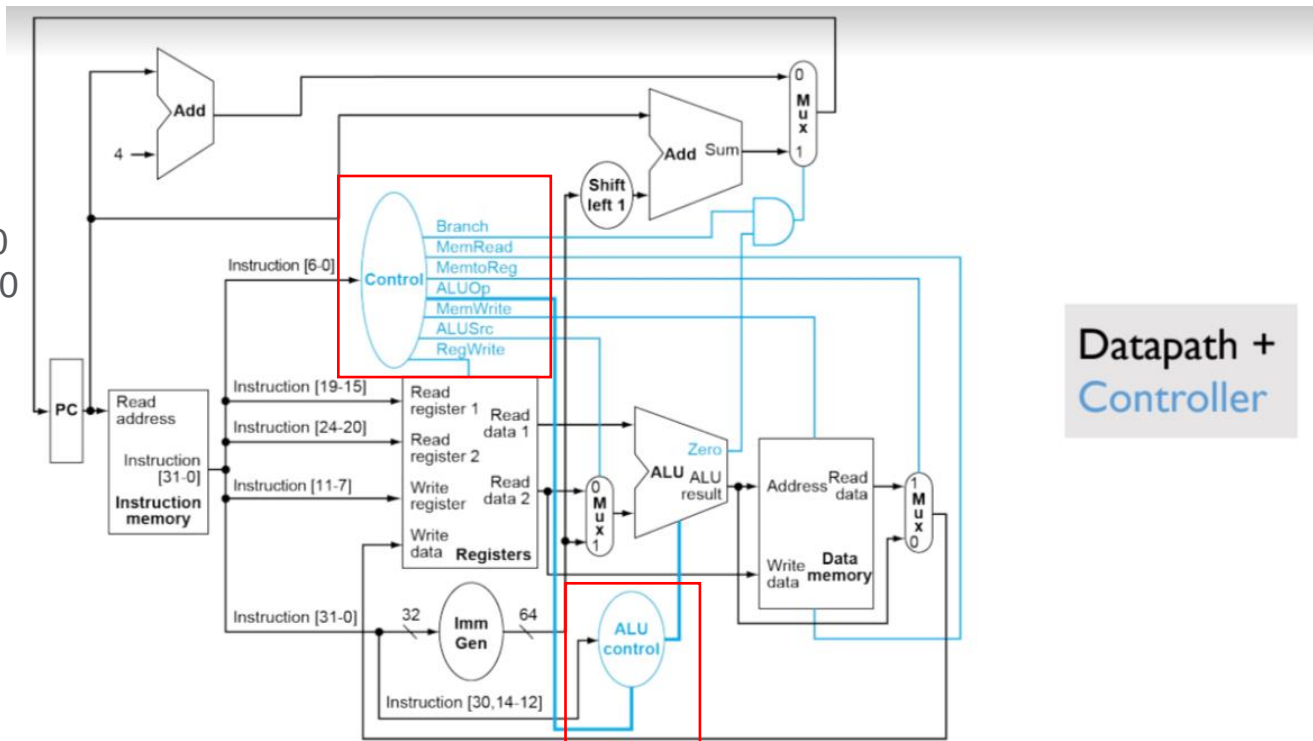

Datapath +  
Controller

\*Images were taken from Hennessy Patterson Book [1].

## Ex) New Instruction?

---

-If one wanted to implement a “swap” instruction, where two register values switch locations, and one needs to use existing instruction types (such as r-type, i-type, etc), what would need to be changed with the existing hardware?

## Ex) New Instruction?

-If one wanted to implement a “swap” instruction, where two register values switch locations, and one needs to use existing instruction types (such as r-type, i-type, etc), what would need to be changed with the existing hardware?

**-Ans:**

- Additional write address
- Additional write port
- Additional reg write control port

